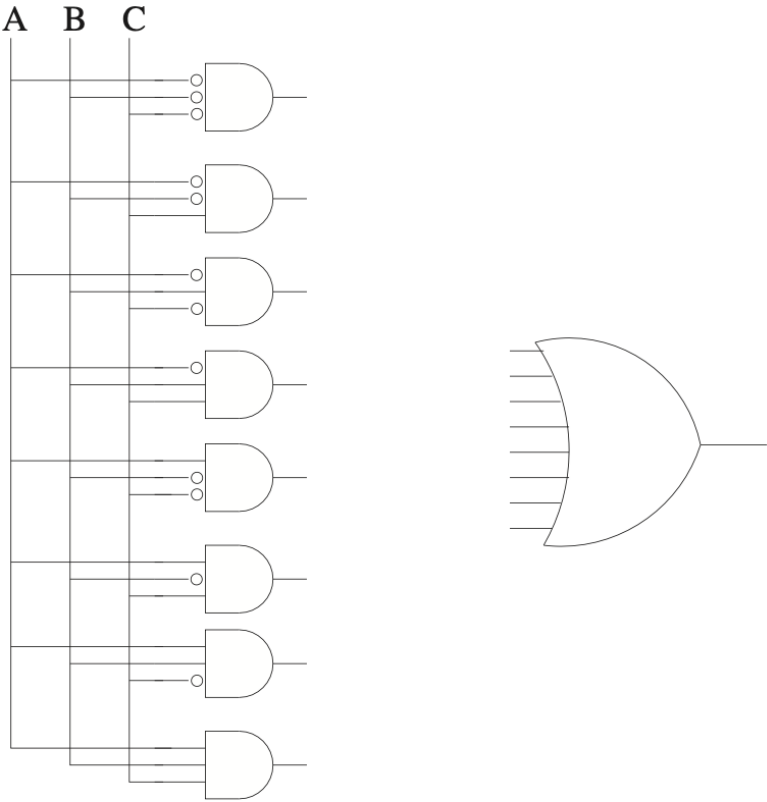





2. 3.12 A function is described by the truth table shown on the left. Your job: Complete the logic implementation shown on the right by adding the appropriate connections.

A	B	C	Out
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



简答题 (2 分) 0 分


附件名  
大小

 image-20210712164330539.png



教师评语:  
不允许添加元件

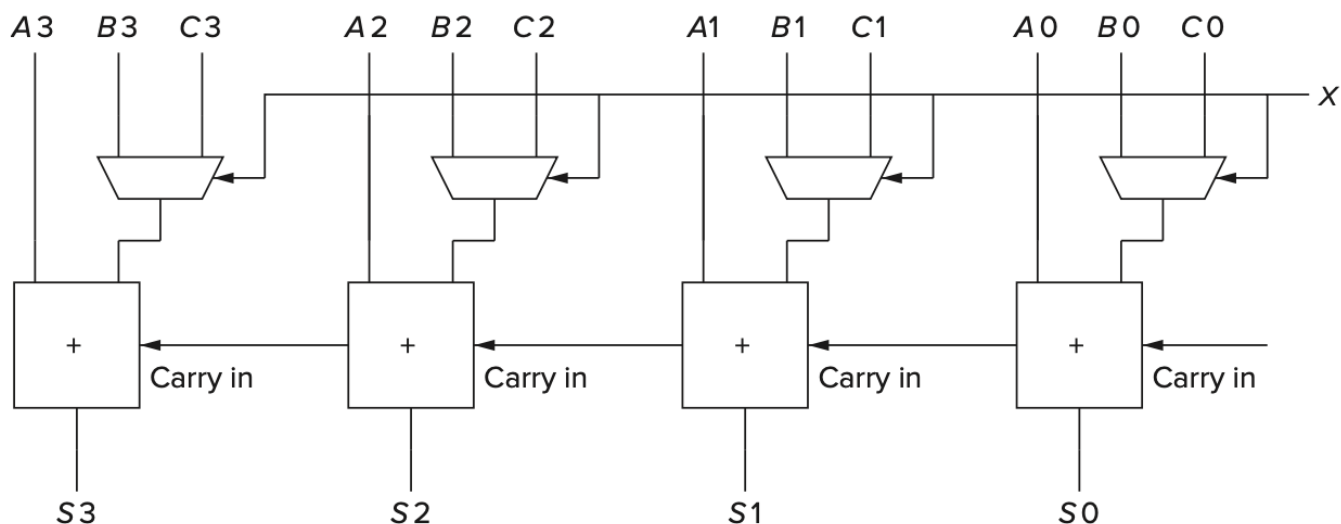3. 3.30 a. Figure 3.42 shows a logic circuit that appears in many of today's processors. Each of the boxes is a full-adder circuit. What does the value on the wire X do? That is, what is the difference in the output of this circuit if  $X = 0$  vs. if  $X = 1$ ?
- b. Construct a logic diagram that implements an adder/subtractor. That is, the logic circuit will compute  $A + B$  or  $A - B$  depending on the value of  $X$ . Hint: Use the logic diagram of Figure 3.42 as a building block.



简答题 (2 分) 1 分

- A. in the circuit , $x = 0$ ; the mux output is  $B_i$ ;  
when  $x = 1$ , the mux output is  $C_i$ .
- B. we will choose  $x = 1$  and get the  $\sim C_i$ ;

附件名  
大小

image-20210712171434599.png

◎

教师评语:  
b中C应该不存在


4. 3.38 Distinguish between a memory address and the memory's addressability.

简答题 (2 分) 2 分

memory address is a address that data located in memory such as 0xFFFF1h.etc  
memory's addressability is number of bit per location.

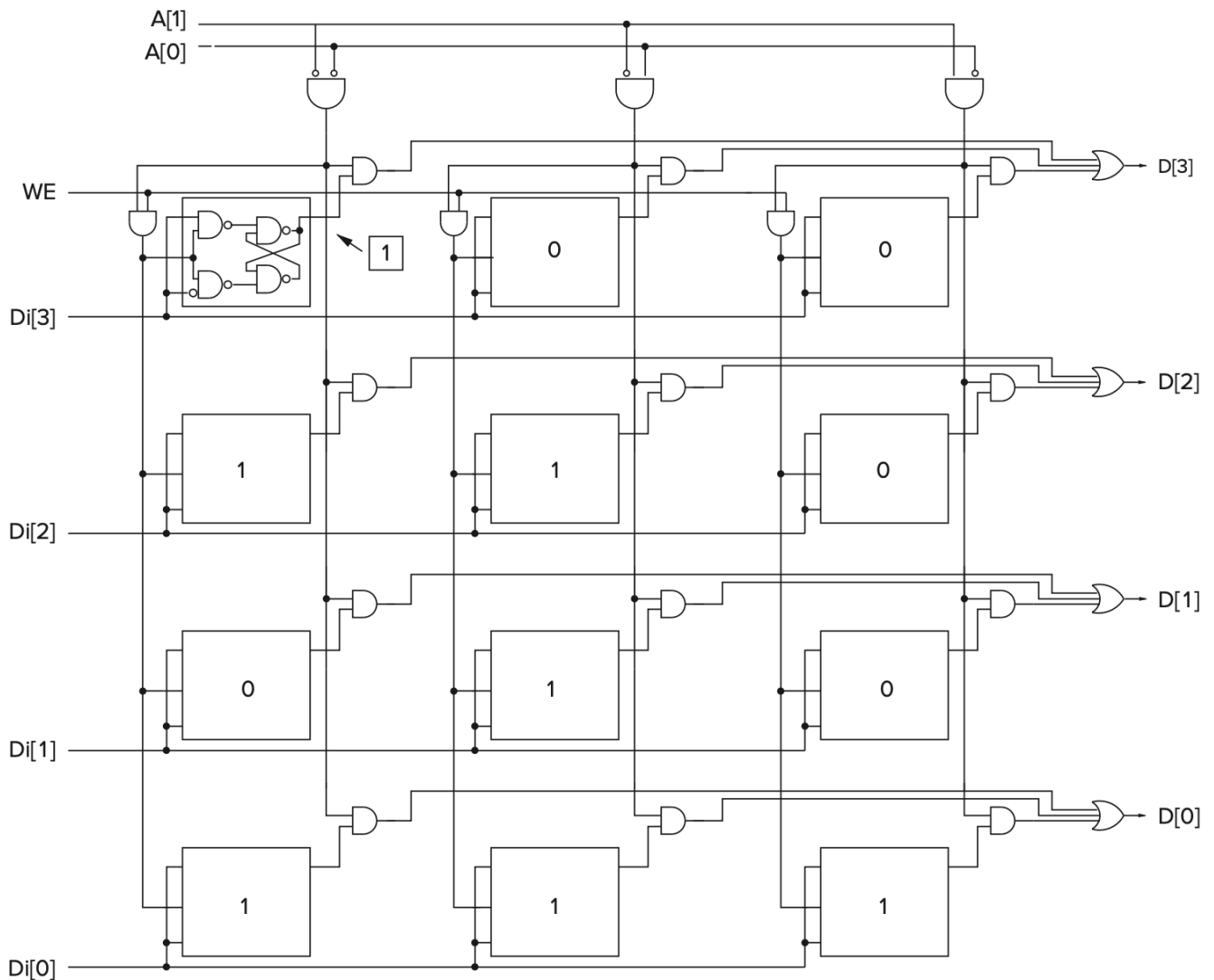5. 3.40 For the memory shown in Figure 3.45:

- What is the address space?
- What is the addressability?
- What is the data at address 2?




简答题 (3分) 3分

- 4
- 4 bit
- 0001'b

6. 3.47 The IEEE campus society office sells sodas for 35 cents. Suppose they install a soda controller that only takes the following three inputs: nickel, dime, and quarter. After you put in each coin, you push a pushbutton to register the coin. If at least 35 cents has been put in the controller, it will output a soda and proper change (if applicable). Draw a finite state machine that describes the behavior of the soda controller. Each state will represent how much money has been put in (Hint: There will be seven of these states). Once enough money has been put in, the controller will go to a final state where the person will receive a soda and proper change (Hint: There are five such final states). From the final state, the next coin that is put in will start the process again.

简答题 (2 分) 1 分

附件名  
大小

 hw.jpg




教师评语:  
缺少回到初始状态

7. 3.50 Prove that the NAND gate, by itself, is logically complete (see Section 3.3.5) by constructing a logic circuit that performs the AND function, a logic circuit that performs the NOT function, and a logic circuit that performs the OR function. Use only NAND gates in these three logic circuits.

简答题 (2 分) 2 分

NOT :  $\text{NAND}(A,A) = \text{NOT}(A)$   
AND :  $\text{NOT}(\text{NAND}(A,B)) = \text{AND}(A,B) = AB$   
OR:  $\text{NOT}(\text{AND}(\text{NAND}(A,A) \text{ NAND}(B,B))) = A+B$

附件名  
大小

 image-20210712164835068.png

